

# DTL - logic gates tutorial / Prof. M.-C. Brunet

①


- Example of a 2-input gate:



The truth table is a summary of all possible input combinations and the corresponding output value. To low voltage corresponds a logic 0; to high voltage corresponds a logic 1.

<u>Truth table</u>		$v_1$	$v_2$	$v_{out}$
		0	0	?
		0	1	?
		1	0	?
		1	1	?

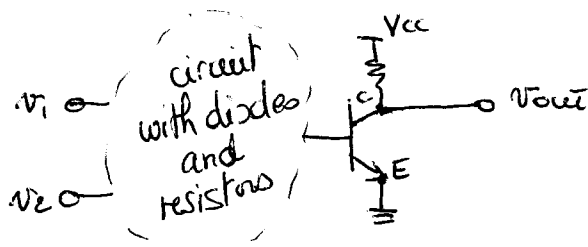- In most DTL gates  $v_{out}$  is  $V_{CE}$  (the output voltage of the Transistor in the circuit) -



- Finding the truth table for  $v_{out}$ : To analyze what the gate is doing consider an input 0V for logic 0, and  $V_{CC}$  (typically 5V) for logic 1. In addition:

- ① if  $v_{out} = \text{low}$ , the BJT is saturated (ON)
  - ② if  $v_{out} = \text{high}$ , the BJT is off (no current is,  $i_c$ )
- } (\*)


one strategy: For each input combination assume

- a state for the BJT (① or ②)
- a state for each diode in the circuit (ON or OFF)

then compute all node voltages in the circuit and currents -

- If there is a contradiction → try other assumptions
- If there is no contradiction → the BJT state defines  $v_{out}$  (see (\*))

• Example (partially solved)

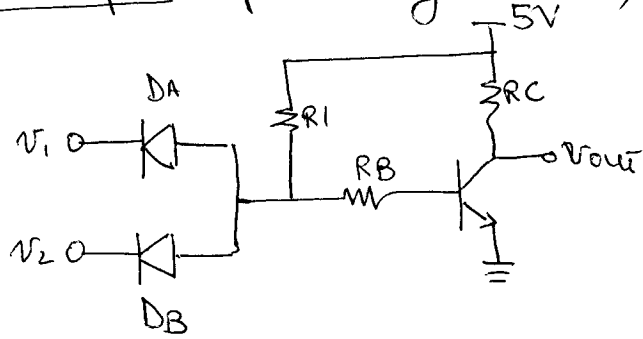


Look at one input combo: ②

$v_1$	$v_2$	$v_{out}$
0	0	
0	1	? ←
1	0	
1	1	

•  $v_1$  is 0: take 0V;  $v_1$  is 1: take 5V

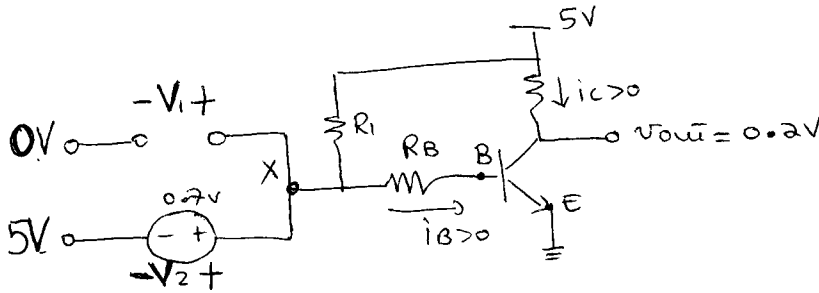Ⓐ) We assume that BJT is ON (saturated), DA is OFF, DB is ON.



(be careful with notations:  $v_1$  and  $V_1$ ,  $v_2$  and  $V_2$  are not the same!)


1) BJT is ON  $\Rightarrow V_{BE} = V_{BEON} = 0.7V$   
 $i_B > 0 \Rightarrow V_X > 0.7V$

2) DB is ON ( $V_2 = 0.7V$ ) and  $V_X - 5 = V_2 \Rightarrow V_X = 5.7V$  ←

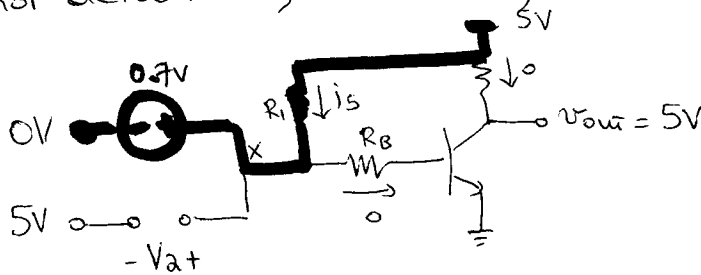3) DA is OFF;  $V_1 = V_X - 0V = 5.7V$  not possible!! (for any diode  $v_d \leq V_{on}$ )

so far no contradiction...

Ⓐ) Assume that BJT is OFF, DA is ON, DB is OFF - This works!! (not detailed; see below).



— current path

$V_X = 0.7V$

$V_2 = 0.7 - 5 = -4.3V$  (off)

$i_S = \frac{5 - V_X}{R_1} = \frac{4.3}{R_1}$

$v_{out} = 5V$

Truth table:

$v_1$	$v_2$	$v_{out}$
0	0	
0	1	1 ←
1	0	
1	1	