

# SP'06

ECE 110

Professors Brunet and Haken

February 13, 2006

## HOUR EXAMINATION #1

Last Name (use capital letters): \_\_\_\_\_

First Name (use capital letters): \_\_\_\_\_

Signature: \_\_\_\_\_

Circle your section: AL1(1pm)-Brunet

BL1(noon)-Haken

**DO NOT TURN THIS PAGE UNTIL YOU ARE TOLD**

Problem	Value	Score
1	10	
2	20	
3	20	
4	10	
5	20	
6	20	
<b>Total</b>	<b>100</b>	

A. Write or print clearly. Answer each problem on the exam itself. If you need extra paper, there is an extra sheet at the end of this exam. Clearly identify the problem number on any additional pages.

B. In order to receive partial or full credit, **you must show all your work**, e.g., your solution process, the equation(s) that you use, the values of the variables used in the equation(s), etc. You must also include the unit of measurement in each answer.


**Students caught cheating on this exam will earn a grade of F for the entire course. Other penalties may include suspension and/or dismissal from the university.**

**Problem 1** (10 points)

For each situation below you must


- draw and label the force  $F$  applied on each wire  
(**HINT**: draw the magnetic field  $B$  first).
- check the one most correct resulting initial motion.

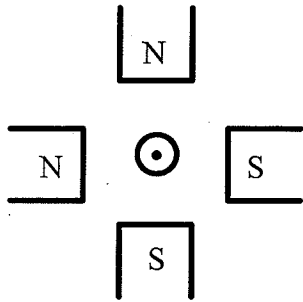i) [5 pts.] (No partial credit will be given for checking one answer without drawing  $F$ .)





- The wire does not move.
- The wire moves up.
- The wire moves left.
- None of the previous answers.

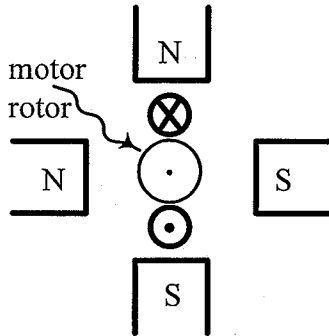ii) [5 pts.] (No partial credit will be given for checking one answer without drawing  $F$ .)




- The rotor does not move.
- The rotor moves clockwise.
- The rotor moves counterclockwise.

**Problem 2 (20 points)**

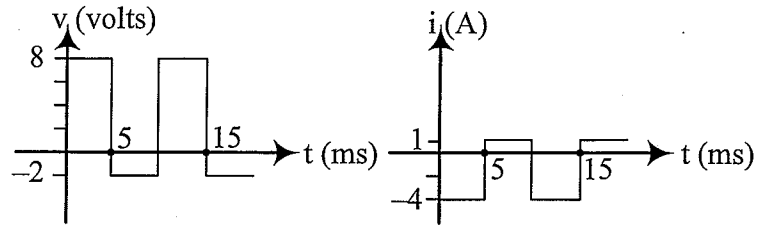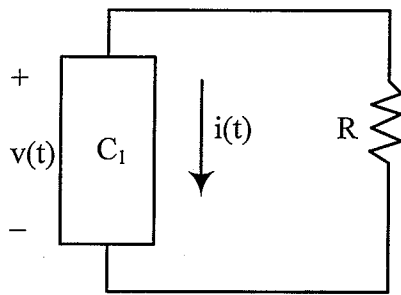

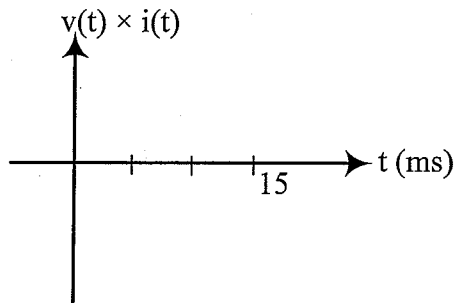i) [5 pts.] Plot  $v(t) \times i(t)$ . Clearly label all points.



ii) [5 pts.] Compute  $A_1 = \text{average}(v(t) \times i(t))$ . Show work.

$A_1 =$

iii) [6 pts.] Compute  $v_{\text{RMS}}$ ,  $i_{\text{RMS}}$ , and  $A_2 = v_{\text{RMS}} \times i_{\text{RMS}}$ . Show work.

$v_{\text{RMS}} =$

$i_{\text{RMS}} =$

$A_2 =$


iv) [4 pts.] Compare  $A_1$  and  $A_2$  (circle one) and give an explanation for the result obtained (i.e., the result was expected; why?).

$A_1 \neq A_2$

Explanation:

$A_1 = A_2$

**Problem 3** (20 points)

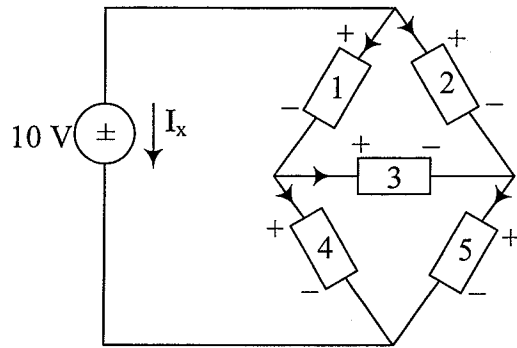

$$i_1 = -1 \text{ A}$$

$$i_4 = 2 \text{ A}$$

$$i_5 = 3 \text{ A}$$

$$v_2 = -4 \text{ V}$$

$$v_3 = 3 \text{ V}$$

i) [4 pts.] How many nodes in this circuit?

ii) [6 pts.] How many independent KCL equations are there for this circuit? Write all the independent KCL equations.


iii) [6 pts.] Write all the independent KVL equations. Use loops that involve the fewest number of voltage drops.

iv) [4 pts.] Solve for  $I_x$  and  $v_4$ .

$$I_x = \boxed{\phantom{000}}$$

$$v_4 = \boxed{\phantom{000}}$$


**Problem 4** (10 points)

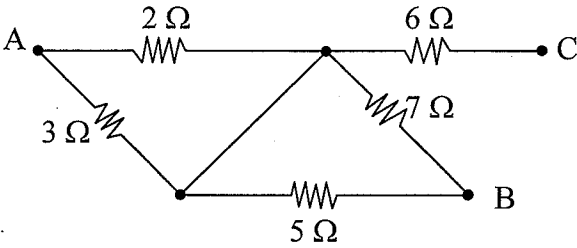

Find  $R_{EQ}$  between A and B. Show all of your work.

$R_{EQ} =$

**Problem 5 (20 points)**

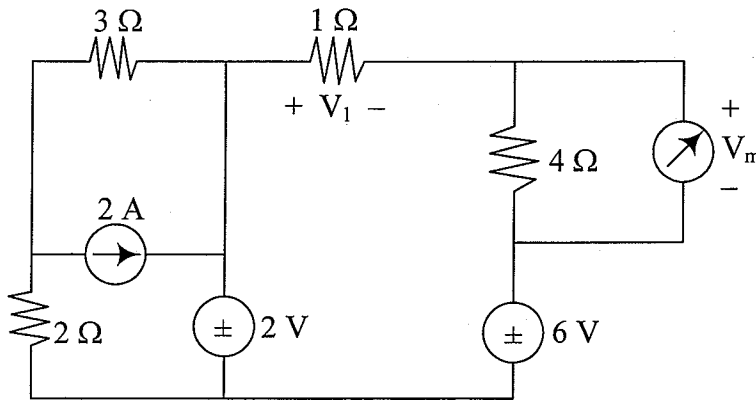

**i) [5 pts.]** How many nodes does the circuit above contain? Label all of them on the circuit.

number of nodes:

**ii) [10 pts.]** Use the voltage divider rule to compute the voltage  $V_m$  measured by the voltmeter. You must first draw below the portion of the circuit (i.e., a set of resistances only) that is used in your computation to apply VDR. Label all nodes using the notations you set in part **i**).


$V_m =$

**iii) [5 pts.]** Deduce  $V_1$  using KVL (write the KVL equation first).


$V_1 =$

**Problem 6 (20 points)**

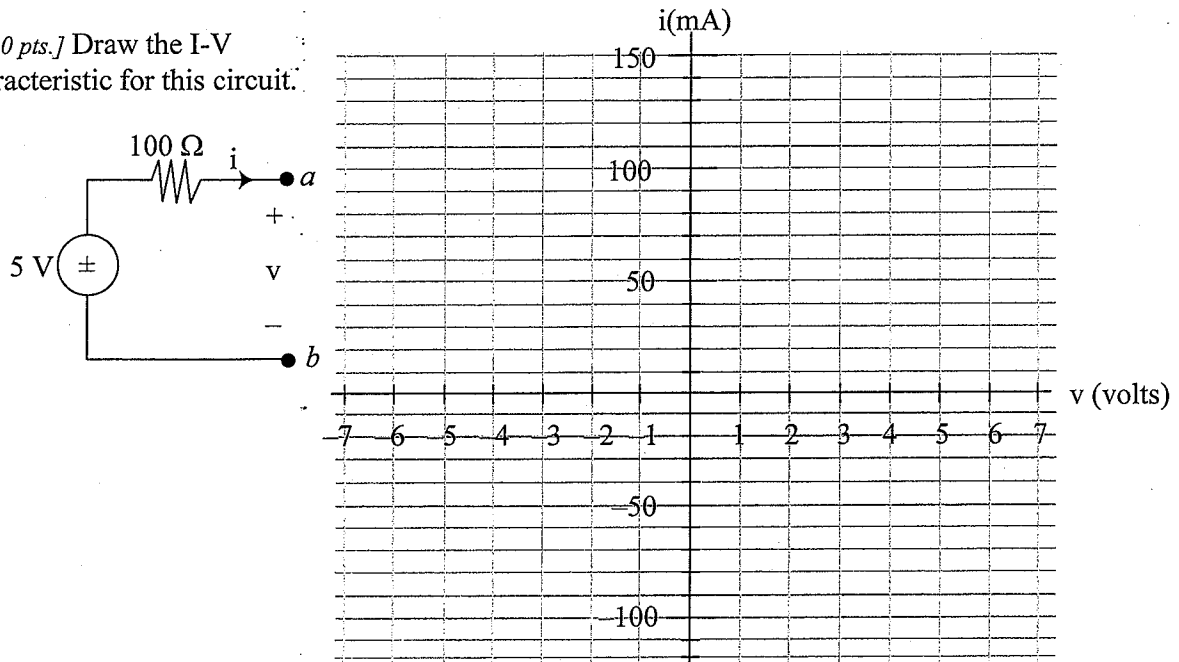
i) [10 pts.] Draw the I-V characteristic for this circuit.



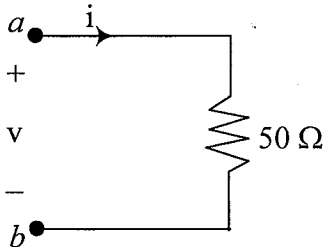ii) [6 pts.] Draw the I-V characteristic for this circuit.



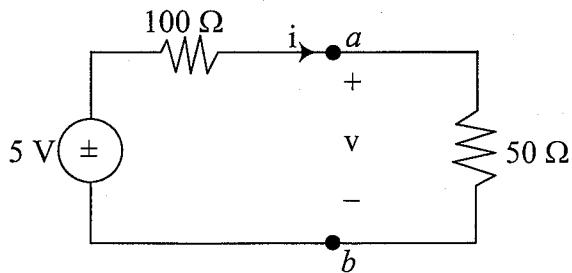iii) [4 pts.] Solve for  $(i, v)$  when the two circuits are connected at  $a$  and  $b$ . Use any method of your choice, but you must show all your work or reasoning.



$i =$

$v =$