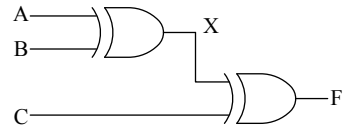


Problem 4 (10 points)

(a) [5 pts.] Complete the truth table for this circuit.



A	B	C	X	F
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

(b) [5 pts.] Assume $G = A_1 \oplus A_2 \oplus \dots \oplus A_7$.

If five of the inputs (among A_1, A_2, \dots, A_7) are equal to 1, then G is equal to

Justify:

Problem 3 (20 points)

a) Convert the Boolean function $F = \overline{\overline{\overline{XY}} \cdot \overline{\overline{X}} \overline{Y}}$ to a SOP form. State the identity or method you used in the conversion.

b) Complete the truth table for the Boolean function in part 3a).

X	Y	F
0	0	
0	1	
1	0	
1	1	


c) For the given truth table, write a Boolean function for it in canonical SOP form.

X	Y	Z	G
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

d) Find the optimal SOP Boolean function for the truth table in 3c).
HINT: The optimal corresponding circuit has 3 gates and 4 inputs. Show your work.

Problem 3 (15 points)

Only the p-mos transistors are shown:

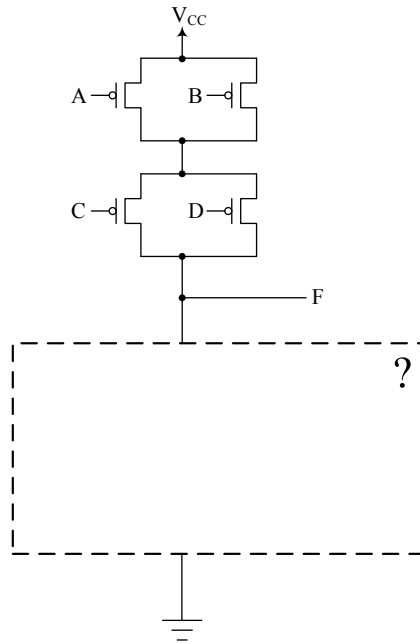

a) [5 pts.] Write a Boolean expression for F. (Hint: Figure out when $F = 1$.)

b) [5 pts.] Deduce a Boolean expression for \bar{F} , then make it SOP form. Show work.


c) [5 pts.] Draw a diagram in the ? above, using all nmos transistors so that the output F is always connected to either V_{CC} or to GND but not both.

Use only nMOS. Draw neatly.

Problem 4 (10 points)

Propose two ways of implementing the Boolean functions below, i.e., two different circuits for each of F and G. Each circuit consists of one gate (do not add gates; simply connect wires by drawing dots on the grid where connections should be). Draw neatly for credit, and show work.

X	Y	F	G
0	0	1	0
0	1	0	0
1	0	1	1
1	1	1	0

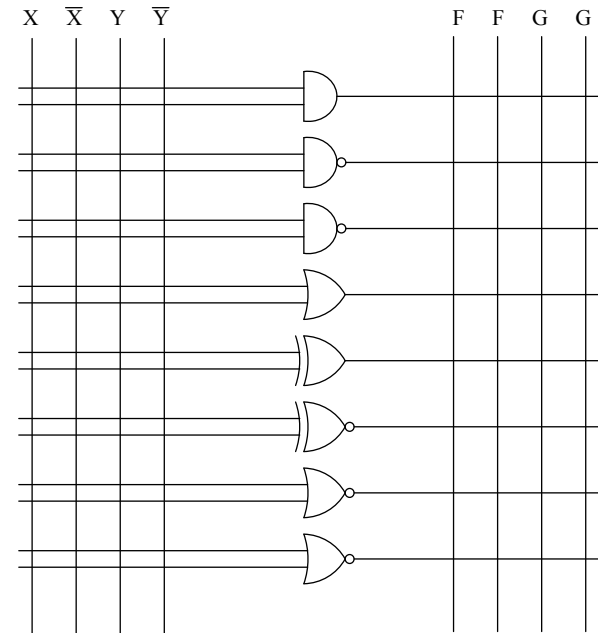


Problem 5 (15 points)

This is the truth table for a Full Adder:



C	A	B	SUM	CARRY
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- a) [5 pts.] Write the canonical SOP for SUM.
- b) [5 pts.] Write the canonical SOP for CARRY, then minimize the SOP. Show work. (HINT: In the resulting optimal AND-OR circuit all the AND gates have only two inputs.)

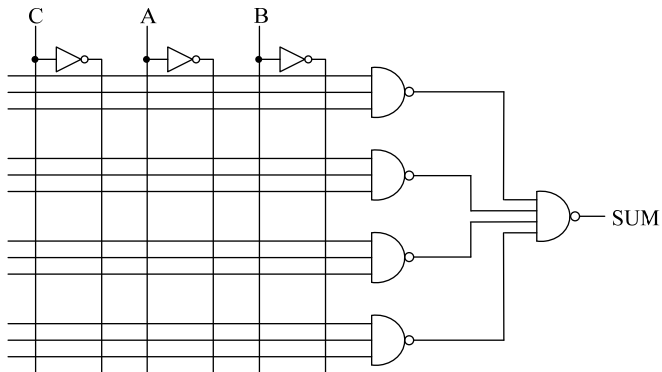- c) [5 pts.] Complete the following for SUM. Draw neatly to get credit. Draw dots on the grid where connections should be.



Problem 3 (20 points)

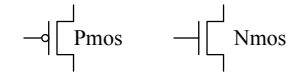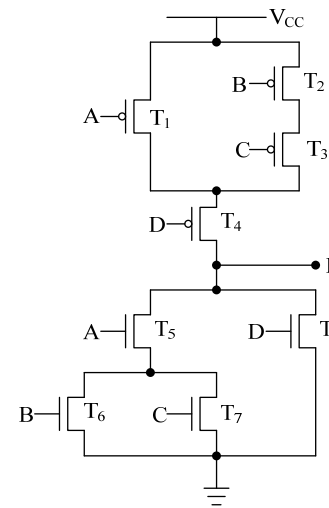

- (a) [5 pts.] Give a Boolean expression with the transistors that must be conducting for F to be equal to 1 [e.g., T₁ and (T₆ or T₄)].

- (b) [5 pts.] State a Boolean expression with the binary values for A, B, C, D so that F is equal to 1 [e.g., A = 0 and (B = 1 or C = 0)].

- (c) [5 pts.] Give the Boolean expression for F corresponding to your statement found in (b).

F (A, B, C, D) =

- (d) [5 pts.] Give an optimal SOP for F.

F (A, B, C, D) =