 


Logic Synthesis

Multi-Level Logic Synthesis

Basic Model: Hardware

Implementing Finite State Machines



$M(X, Y, S, S_0, \delta, \lambda)$:

X : Inputs

Y : Outputs

S : Current State

S_0 : Initial State(s)


δ : $X \times S \rightarrow S$ (next state function)

λ : $X \times S \rightarrow Y$ (output function)

Delay element:

- Clocked: synchronous
 - single-phase clock, multiple-phase clocks
- Unclocked: asynchronous

General Logic Structure

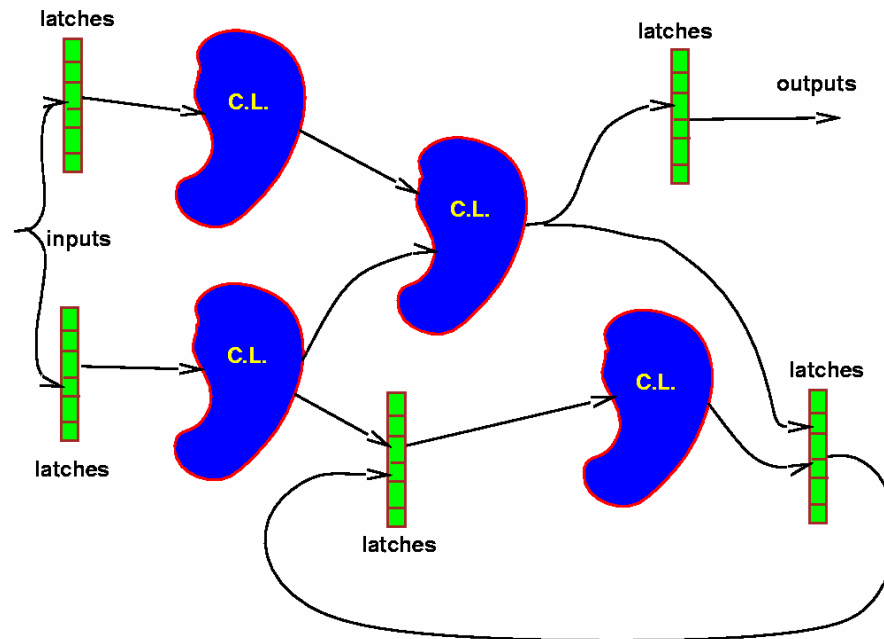

- Combinational optimization
 - keep latches/registers at current positions, keep their function
 - optimize combinational logic in between
- Sequential optimization
 - change latch position/function


Optimization Criteria for Synthesis

The optimization criteria for multi-level logic is to *minimize* some function of:


1. Area occupied by the logic gates and interconnect (approximated by literals = transistors in technology independent optimization)
2. Critical path delay of the longest path through the logic
3. Degree of testability of the circuit, measured in terms of the percentage of faults covered by a specified set of test vectors for an approximate fault model (e.g., single or multiple stuck-at faults)
4. Power consumed by the logic gates
5. Noise immunity
6. Placeability, Wireability
7. Manufacturability

while simultaneously satisfying upper or lower bound constraints placed on these physical quantities


Example: Area-Delay Trade-off

 

Two-Level (PLA) vs. Multi-Level

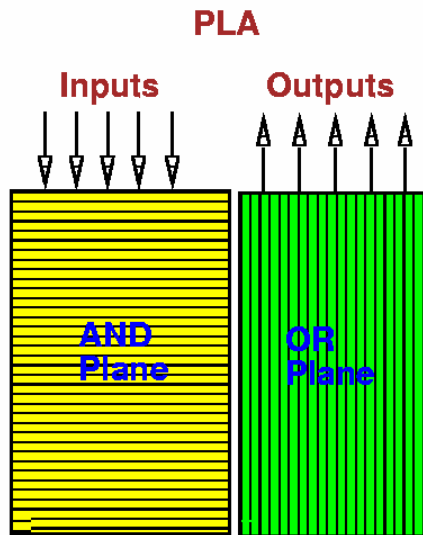

E.g. Standard Cell Layout

 

PLA

- control logic
- constrained layout
- highly automatic
- technology independent
- multi-valued logic
- input, output, state encoding

Very predictable

Multi-level Logic

- all logic
- general (e.g. standard cell, regular blocks,..)
- automatic
- partially technology independent
- some ideas
- part of multi-level logic

Very hard to predict

General Approaches to Synthesis

- **PLA Synthesis:**
 - theory well understood
 - predictable results in a top-down flow
- **Multi-Level Synthesis:**
 - optimization criteria very complex
 - except niches, no general theory available
 - greedy optimization approach
 - incrementally improve along various dimensions of the criteria
 - works on common design representation (circuit or network representation)
 - attempt a change, accept if criteria improves, otherwise reject

Transformation-based Synthesis

- all modern synthesis systems are build that way
 - set of transformations that change network representation
 - work on uniform network representation
 - “script” of “scenario” that can combine those transformations to a overall greedy
- transformations differ in:
 - the scope they are applied
 - local scope versus global restructuring
 - the domain they optimize
 - combinational versus sequential
 - timing versus area
 - technology independent versus technology dependent
 - the underlying algorithms they use
 - BDD based, SAT based, structure based

Network Representation


Boolean network:

- directed acyclic graph (DAG)
- node logic function representation $f_j(x, y)$
- node variable y_j : $y_j = f_j(x, y)$
- edge (i, j) if f_j depends explicitly on y_i


Inputs $x = (x_1, x_2, \dots, x_n)$

Outputs $z = (z_1, z_2, \dots, z_p)$

 External don't cares $d_1(x), d_2(x), \dots, d_p(x)$



Typical Synthesis Scenario

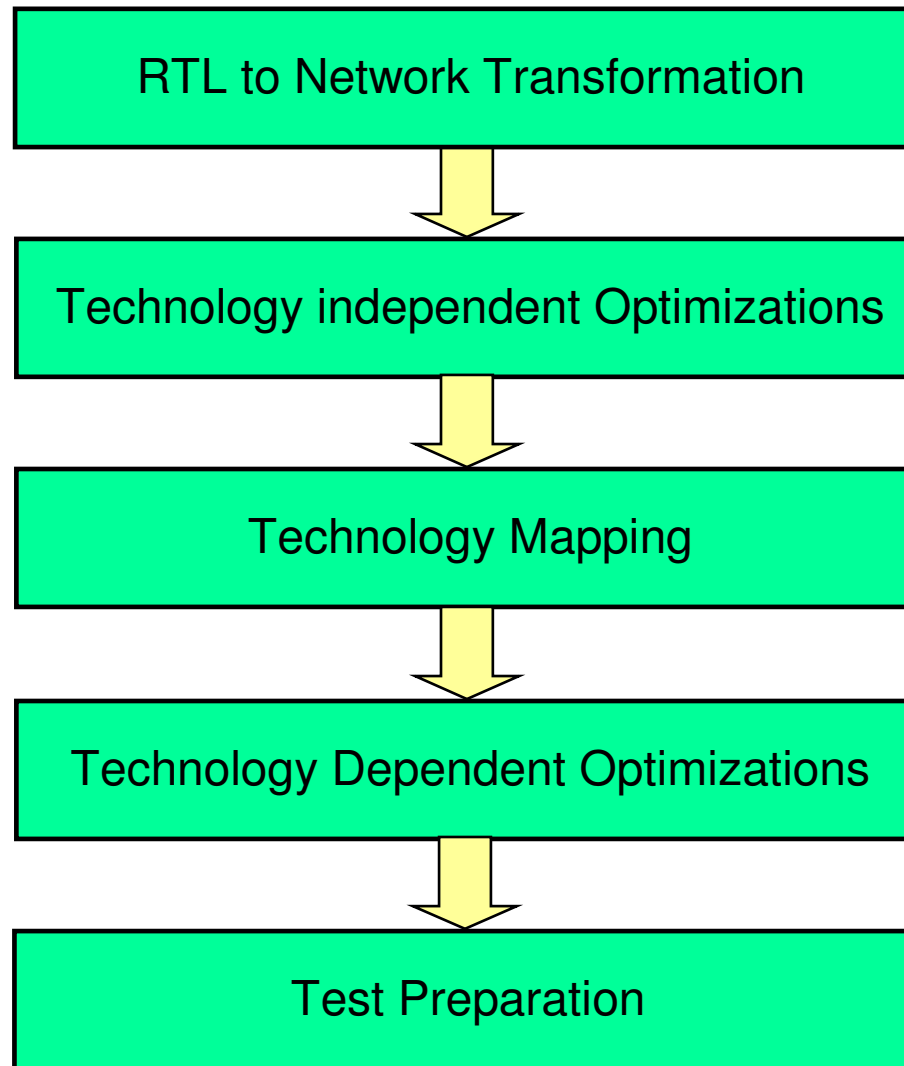

- read Verilog
- control/data flow analysis
- basic logic restructuring
- crude measures for goals
- use logic gates from target cell library
- timing optimization
- physically driven optimizations
- improve testability
- test logic insertion

Local versus Global Transformations

- Local transformations optimize the function of one node of the network
 - smaller area
 - faster performance
 - map to a particular set of cells
- Global transformations restructure the entire network
 - merging nodes
 - spitting nodes
 - removing/changing connections between nodes
- Node representation:
 - SOP, POS
 - BDD
 - Factored forms
 - keep size bounded to avoid blow-up of local transformations

Sum of Products (SOP)

Example:

$$abc'+a'bd+b'd'+b'e'f \text{ (sum of cubes)}$$

Advantages:

- easy to manipulate and minimize
- many algorithms available (e.g. AND, OR, TAUTOLOGY)
- two-level theory applies

Disadvantages:


- Not representative of logic complexity. For example

$$f=ad+ae+bd+be+cd+ce \quad f'=a'b'c'+d'e'$$

These differ in their implementation by an **inverter**.

- hence not easy to **estimate** logic; difficult to estimate **progress** during logic manipulation

Reduced Ordered BDDs

 

- like factored form, represents both function and complement
- like network of muxes, but restricted since controlled by primary input variables
 - not really a good estimator for implementation complexity
- given an ordering, reduced BDD is canonical, hence a good replacement for truth tables
- for a good ordering, BDDs remain reasonably small for complicated functions (e.g. not multipliers)
- manipulations are well defined and efficient
- true support (dependency) is displayed

Factored Forms

Example: $(ad+b'c)(c+d'(e+ac'))+(d+e)fg$

Advantages

- good representative of logic **complexity**
 $f=ad+ae+bd+be+cd+ce \quad f'=a'b'c'+d'e' \Rightarrow f=(a+b+c)(d+e)$
- in many designs (e.g. complex gate CMOS) the **implementation** of a function corresponds directly to its factored form
- good **estimator** of logic implementation complexity
- doesn't **blow up** easily

Disadvantages

- not as many algorithms available for **manipulation**
- hence often just **convert** into SOP before manipulation