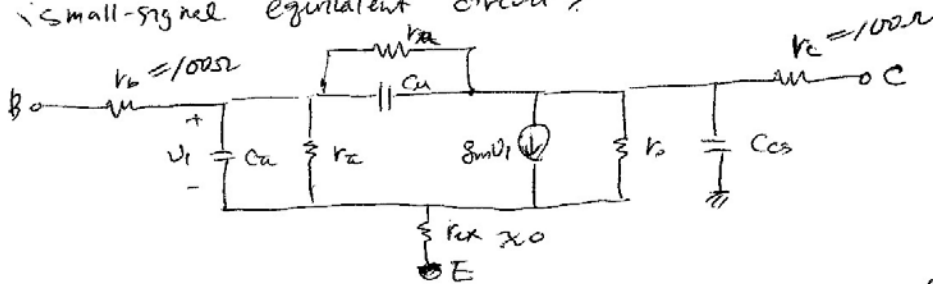


1.11 npn transistor

- $r_b = 100 \Omega$, $r_c = 100 \Omega$, $\beta_0 = 100$, $r_o = 50 k\Omega$ @ $I_c = 1 mA$... ③
- $\psi_0 = 0.55 V$
- C_{je} is constant in the forward-bias region
- $r_M = 5\beta_0 r_o$
- $f_T = 600 MHz$ @ $I_c = 1 mA$, $V_{CB} = 10 V$... ①
- $f_T = 1 GHz$ @ $I_c = 10 mA$, $V_{CB} = 10 V$... ②
- $C_M = 0.15 pF$ @ $V_{CB} = 10 V$
- $C_{cs} = 1 pF$ @ $V_{CS} = 10 V$

(small-signal equivalent circuit)



• for τ_F and C_{je} , from ① and ②

• for V_A , from ③

$$\begin{cases} \frac{1}{2\pi \cdot 600M} = \tau_F + \frac{V_T}{1mA} C_{je} + \frac{V_T}{1mA} C_M \\ \frac{1}{2\pi \cdot 1G} = \tau_F + \frac{V_T}{10mA} C_{je} + \frac{V_T}{10mA} C_M \end{cases}$$

$C_M = 0.15 pF$, $V_T = 0.026$

$\Rightarrow \tau_F = 147 ps$, $C_{je} = 4.4 pF$

$$V_A = r_o I_c = 50 V$$

(a) $I_c = 0.1 mA$

$$g_m = \frac{I_c}{V_T} = 3.8 mA/V$$

$$r_a = \frac{\beta_0}{g_m} = 26 k\Omega$$

$$r_o = \frac{V_A}{I_c} = 500 k\Omega$$

$$r_M = 5\beta_0 r_o = 250 M\Omega$$

$$C_a = C_b + C_{je} = \tau_F g_m + C_{je} = 5.0 pF$$

$$C_M = 0.15 pF \sqrt{\frac{1 - \frac{V_0}{0.55}}{1 - \frac{2}{0.55}}} = 0.31 pF$$

$$C_{cs} = 1 pF \sqrt{\frac{1 - \frac{V_0}{0.55}}{1 - \frac{15}{0.55}}} = 0.82 pF$$


$\frac{0.1k}{= m_s} = 0.5$ are used.

	$I_c = 1 mA$	$I_c = 5 mA$
g_m	38 mA/V	190 mA/V
r_a	2.6 k Ω	530 Ω
r_o	50 k Ω	10 k Ω
r_M	25 M Ω	5 M Ω
$C_a = C_b + C_{je}$	10 pF	32.4 pF
C_M	0.31 pF	0.31 pF
C_{cs}	0.82 pF	0.82 pF

$$(b) \quad f_T = \frac{1}{2\pi \left(\tau_F + \frac{C_{je}}{g_m} + \frac{C_{je}}{g_m} \right)} = \frac{1}{2\pi \left\{ \tau_F + \frac{V_T}{I_C} (C_{je} + C_{cu}) \right\}}$$

When $\frac{V_T}{I_C} (C_{je} + C_{cu}) \gg \tau_F$, $f_T \cong \frac{I_C}{2\pi V_T (C_{je} + C_{cu})} \Rightarrow \left. \begin{array}{l} I_C \\ 1 \mu A \\ \end{array} \right\} f_T$

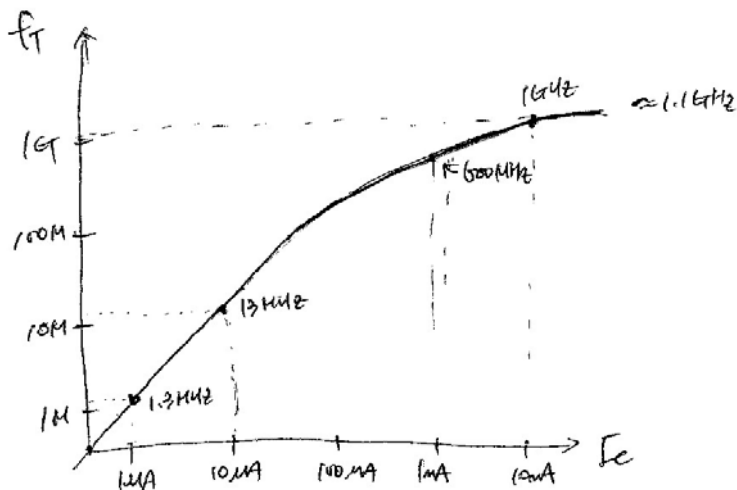When $\frac{V_T}{I_C} (C_{je} + C_{cu}) \ll \tau_F$, $f_T \cong \frac{1}{2\pi \tau_F} \approx 1.1 \text{ GHz}$.



1.15. NMOS

$W = 10 \mu$ $L = 1 \mu$ $K' = 104 \mu A/V^2$ $\lambda = 0.024 V^{-1}$ $t_{ox} = 80 \text{ \AA}$

$\phi_f = 0.3 V$ $V_{t0} = 0.6 V$ $N_A = 5 \times 10^{15}$

(a) $V_t = 0.6$


$\frac{K'}{2} \cdot \frac{W}{L} = 97 \times 10 = 970 \mu A/V^2$

In the triode region

$I_D = 0.97 [2 \times (V_{GS} - 0.6) V_{DS} - V_{DS}^2]$ mA

In the saturation region

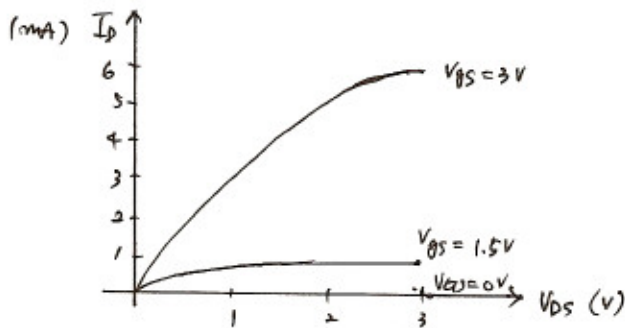$I_D = 0.97 (V_{GS} - 0.6)^2 (1 + 0.024 V_{DS})$ mA




(b) $r = \frac{1}{C_{ox}} \sqrt{2q \epsilon N_A} = 0.095 \sqrt{V}$


$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = 4.3 \text{ fF}/\mu m^2$

$V_t = V_{t0} + r (\sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f})$

V_{SB}	0V	0.5V	1V
V_t	0.6V	0.626V	0.647V

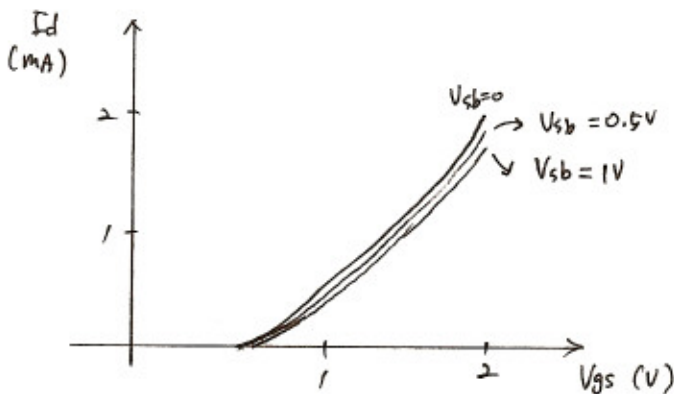

1.16

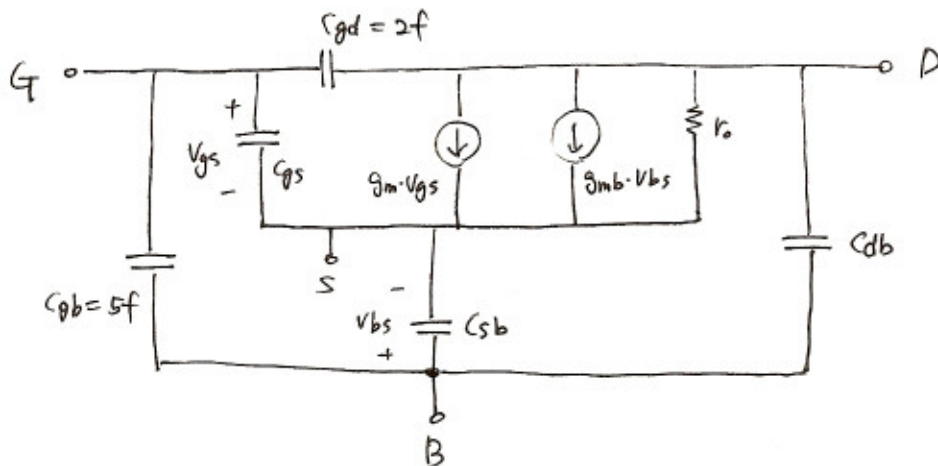

$$V_t = 0.647 \text{ V}$$

$$I_D = \frac{k'}{2} \cdot \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS}) = 127 \mu\text{A}$$

$$g_m = \frac{2I_D}{V_{GS} - V_t} = 720 \mu\text{A/V}$$

$$g_{mb} = \frac{r \cdot g_m}{2\sqrt{2\beta_f + V_{SB}}} = 27 \mu\text{A/V}$$

$$r_o = \frac{1}{\lambda I_D} \approx 327 \text{ k}\Omega$$

$$C_{sb} = \frac{C_{sb0}}{\sqrt{1 + \frac{V_{SB}}{V_0}}} = 12.8 \text{ f}$$

$$C_{db} = \frac{C_{db0}}{\sqrt{1 + \frac{V_{DB}}{V_0}}} = 8.7 \text{ f}$$

$$C_{gs} = \frac{2}{3} C_{ox} W L + 2 \text{ f} = 30.7 \text{ f}$$